
## Active Attenuator Schematic

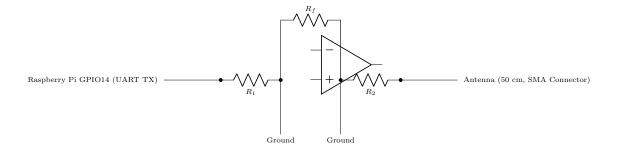

## Schematic Legend

Symbol	Description
pi	Raspberry Pi GPIO14 (UART TX)
res1	Input Resistor (R1)
opamp_in	Operational Amplifier Input
opamp_out	Operational Amplifier Output
res2	Output Resistor (R2)
ant	Antenna (50 cm, SMA Connector)
gnd1	Ground (for input side)
gnd2	Ground (for output side)

## Component Values

Symbol	Description	Value/Formulas
$R_1$	Input Resistor	$1 \text{ k}\Omega$
$R_2$	Output Resistor	$1~\mathrm{k}\Omega$
$R_f$	Feedback Resistor	$31.6 \text{ k}\Omega$ for 30 dB, 100 k $\Omega$ for 40 dB